

# 國立成功大學工程科學系

## 電子學第二次作業

2023/3/18

繳交日期：2023/3/30

1. Fig. 1 shows a weighted summer circuit using an ideal op amp has three inputs resistors and a feedback resistor of  $40\text{ k}\Omega$ . A signal  $v_1$  is connected to two of the inputs while a signal  $v_2$  is connected to the third input. Express  $v_o$  in terms of  $v_1$  and  $v_2$ . If  $v_1 = 1\text{ V}$  and  $v_2 = -1\text{ V}$ , what is  $v_o$ ?

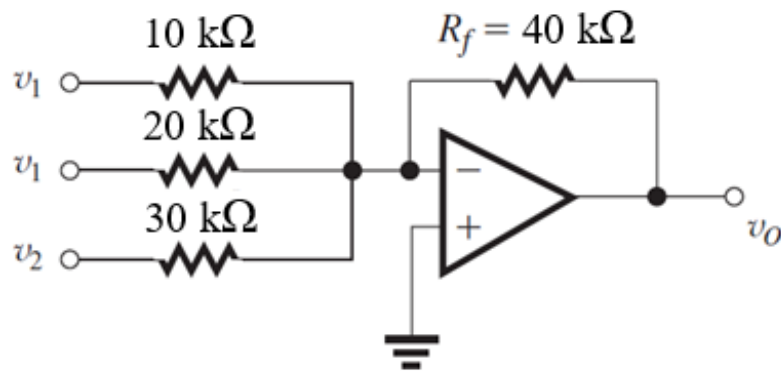


Fig. 1

2. For the circuit in Fig. 2, assuming an ideal op amp, find the currents through all branches (2, 3, 5, 6) and the voltages at all nodes (1, 4).

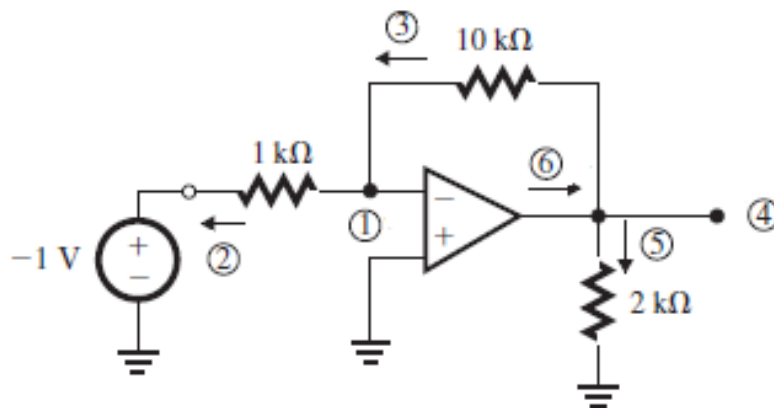


Fig. 2

3. For the circuit in Fig. 3,  $R_1 = R_3 = 5 \text{ k}\Omega$  and  $R_2 = R_4 = 100 \text{ k}\Omega$ . Find the differential voltage gain  $A_d \equiv v_o/v_{id}$  and differential input resistance  $R_{id}$ . If the resistance ratios  $(R_2/R_1)$  and  $(R_4/R_3)$  are different from each other by 1%, what do you expect the common-mode gain  $A_{cm} \equiv v_o/v_{lcm}$  to be?

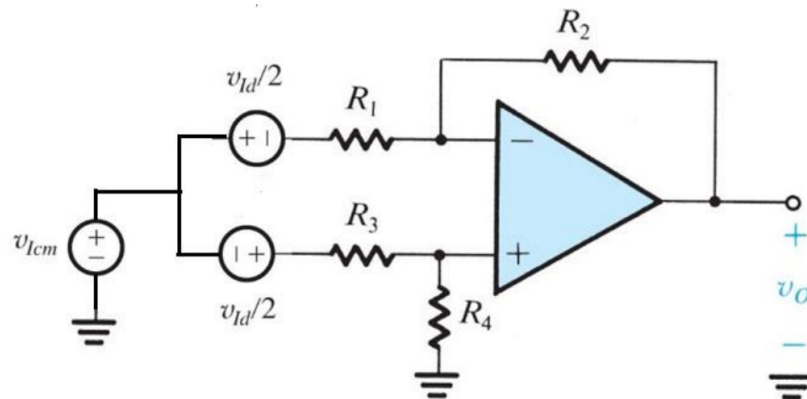


Fig. 3

4. The circuit in Fig. 4 utilizes an ideal op amp.
- Find  $I_1$ ,  $I_2$ ,  $I_3$ ,  $I_L$ , and  $V_x$ .
  - If  $V_O$  is not to be lower than  $-13 \text{ V}$ , find the maximum allowed value for  $R_L$ .
  - If  $R_L$  is varied in the range  $100 \text{ }\Omega$  to  $1 \text{ k}\Omega$ , what is the corresponding change in  $I_L$  and in  $V_O$ ?

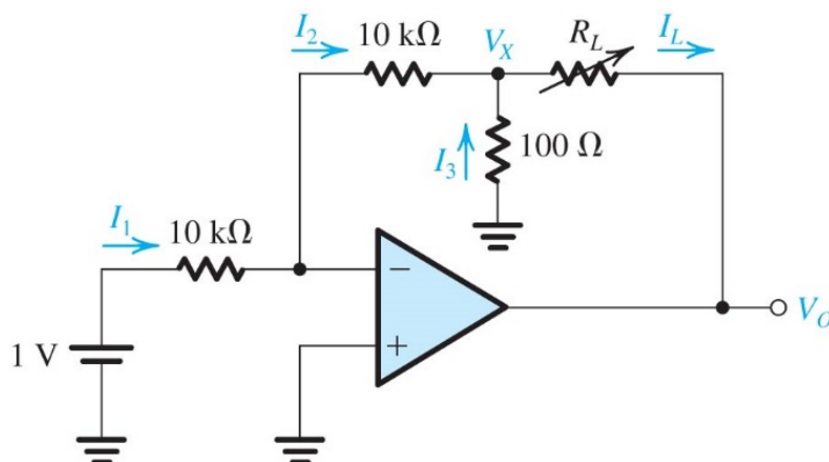


Fig. 4

5. For the circuit shown in Fig. 5, a circuit that performs a low pass STC function. Such a circuit is known as a first-order, low-pass active filter. Derive the transfer function and show that the dc gain is  $(-R_2/R_1)$  and the 3-dB frequency  $\omega_0 = 1/CR_2$ . Design the circuit to obtain an input resistance of 10 k $\Omega$ , a dc gain of 40 dB, and a 3-dB frequency of 1 kHz. At what frequency does the magnitude of the transfer function reduce to unity?

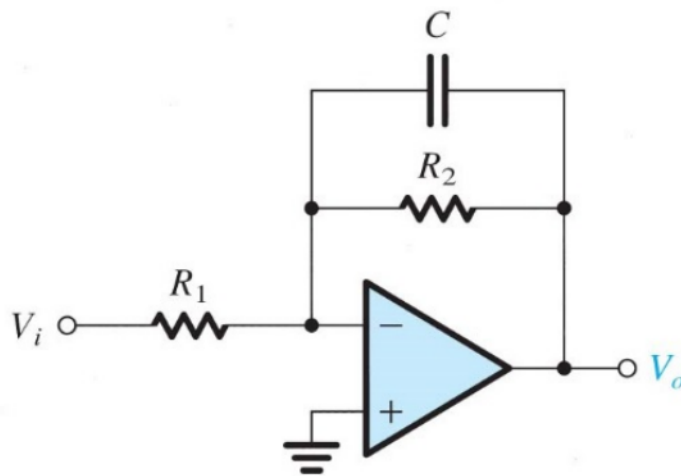


Fig. 5